
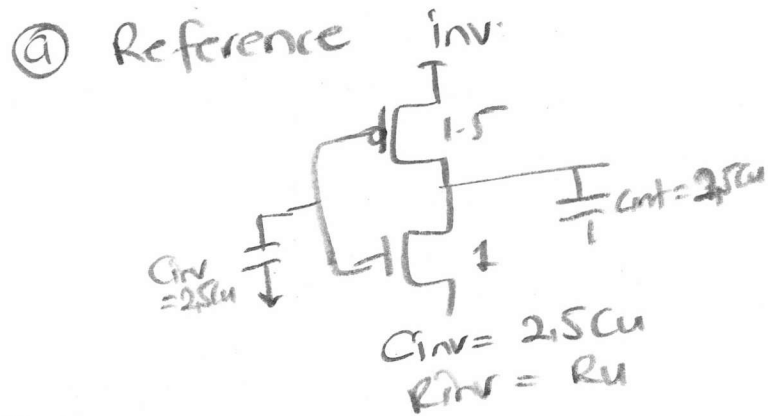


## Homework #4

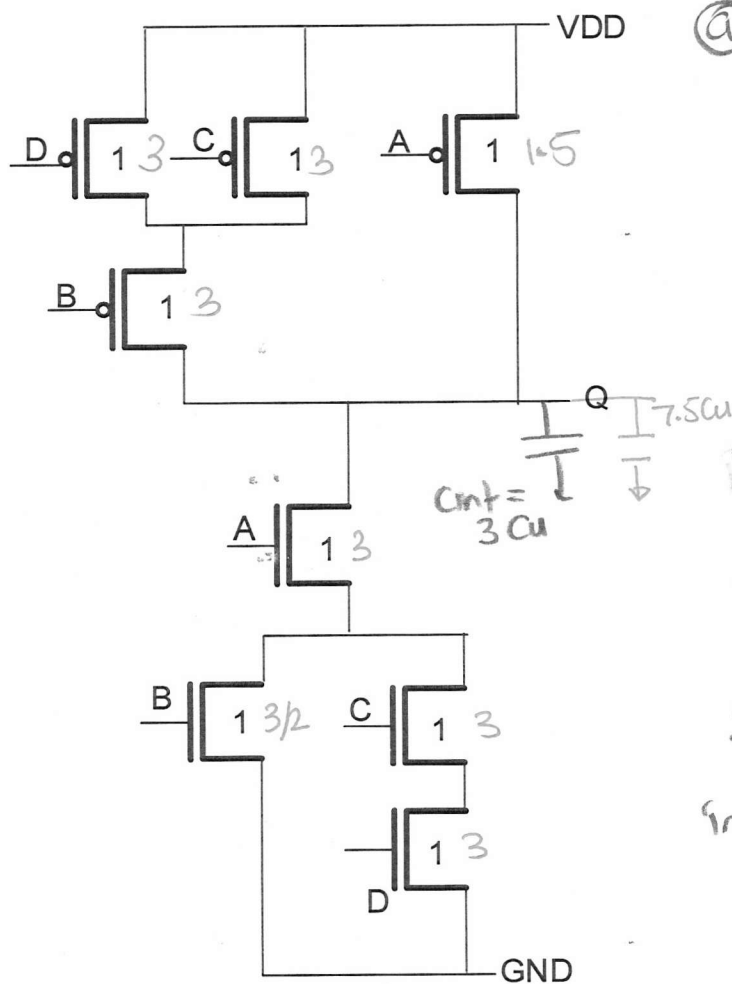Q1. A complex gate is given in the Figure where  $\mu_n/\mu_p=1.5$ .

- Determine  $p_A$ ,  $p_B$ ,  $g_A$ ,  $g_B$  for this gate given the sizing of the transistors.
- Re-size the transistors such that the resistance of pull-up and pull-down paths equals to unit resistance.
- Determine  $p_A$ ,  $p_B$ ,  $g_A$ ,  $g_B$  for this gate given your sizes from part (b).



inp A  
worst case resistance  $3R_u$

$$p_A = \frac{3R_u}{R_u} \times \frac{3C_u}{2.5C_u} = 3.6$$

$$g_A = \frac{3R_u}{R_u} \times \frac{2C_u}{2.5C_u} = 2.4$$

inp B  
 $R_E = 3R_u$  (PMOS path)

$$p_B = \frac{3R_u}{R_u} \times \frac{3C_u}{2.5C_u} = 3.6$$

$$g_B = \frac{3R_u}{R_u} \times \frac{2C_u}{2.5C_u} = 2.4$$


②  $p_A = \frac{7.5C_u}{2.5C_u} = 3$

$$g_A = \frac{4.5C_u}{2.5C_u} = 1.8$$


$$p_B = \frac{7.5C_u}{2.5C_u} = 3$$

$$g_B = \frac{4.5C_u}{2.5C_u} = 1.8$$

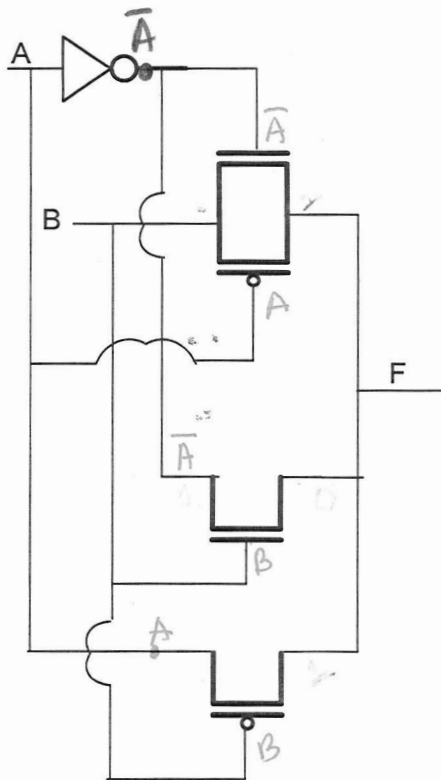
Q2. Three TG logic circuits are given below. Determine the truth table in the space given. If there is a contention, write X.



A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

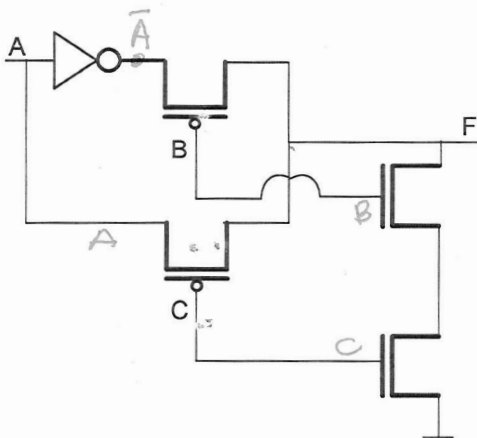


A	B	C	F
0	0	0	X
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	X
1	0	1	0
1	1	0	1
1	1	1	0

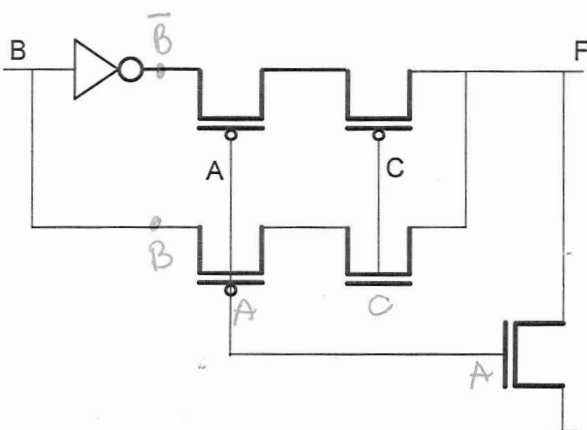

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Q3

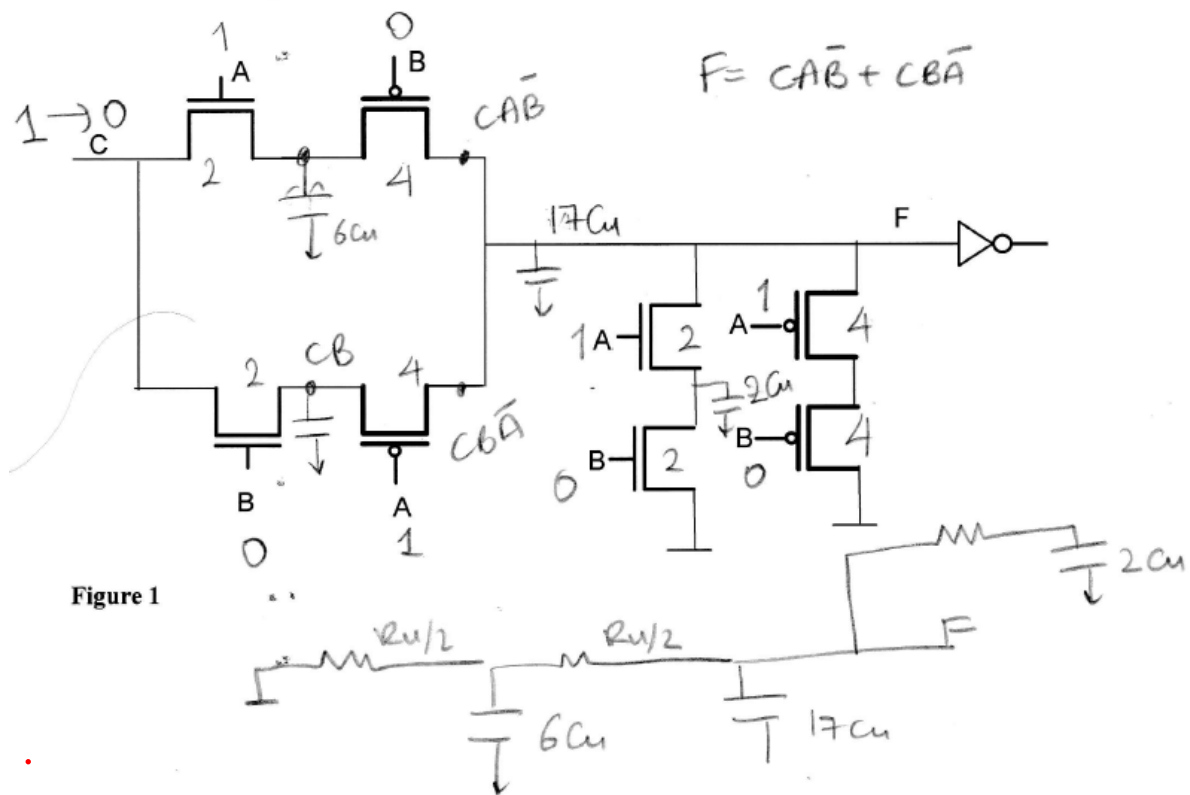


$$T = \frac{R_u}{2} (25C_u) + \frac{R_u}{2} (19C_u) = 22 R_u C_u$$

$$t_d = 15 R_u C_u$$

**Q3.** A PG circuit is given in the Figure. Threshold voltage for transistors is 0.6V. Supply voltage is 2.5V.

- Determine the logic function, F
- Assuming A, B, C are primary inputs, size the transistors such that all paths from output to GND/VDD have  $R_u$  resistance.  $\mu_n/\mu_p=2$
- Draw the Elmore model for ABC: 101→100
- Determine the delay for ABC: 101→100 in terms of  $R_u$ ,  $C_u$ .
- Find the voltage at node F for:


ABCX	V <sub>F</sub>
000	0.6V
110	0
011	1.9V
100	0.6V

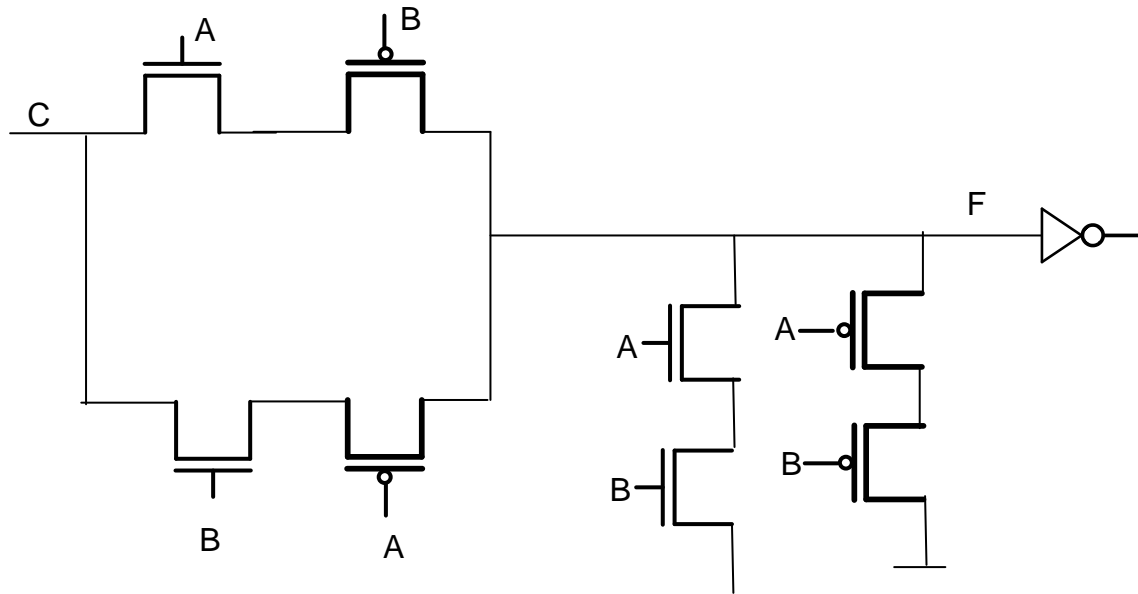

Q4.

(a)

segment 1

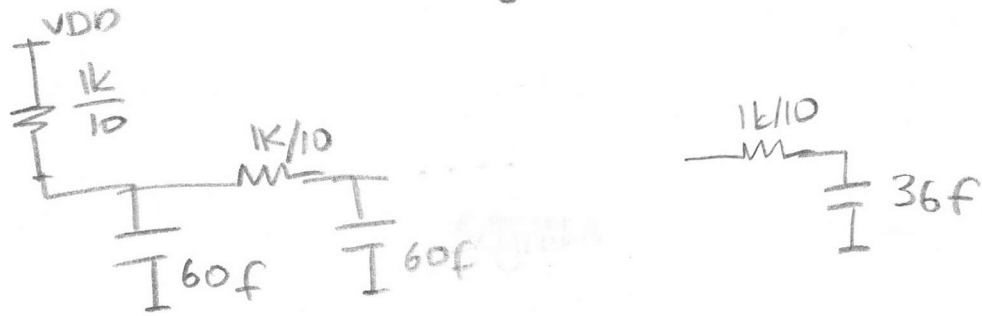


$$\tau_i = 36f \times 1k + 60f \times 0.9k + 60f \times 0.8k + \dots + 60f \times 0.1k$$

$$\tau_i = 36ps + 60ps(0.9 + 0.8 + 0.7 + \dots + 0.1)$$

$\frac{9 \times 10}{2} = 4.5$

$$\tau_i = 306ps$$

Segment with Load

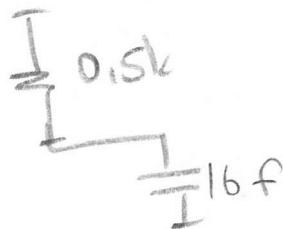


$$\tau_2 = 8ps$$

(this segment does not change)

$$\tau = 314ps \quad t = 220ps$$


⑥ 4 segments

First 2

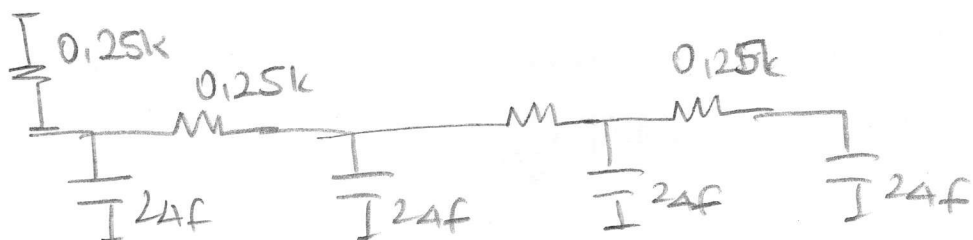

$$\tau_1 = \tau_2 = 0.25k \times 24f (4+3+2+1) = 60ps$$

3rd segment

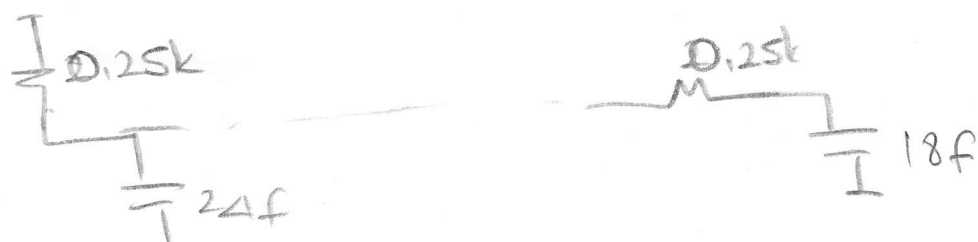

$$\tau_3 = 18f \times 1k + 24f \times (0.75k + 0.50k + 0.25k) = 54ps$$

4th segment identical to part (a)

$$\tau = (2 \times 60 + 54 + 8)ps = 182ps$$

$$t = 127.4ps$$