

# HW4 Solutions

① Amortized wafer cost

$$= \frac{5000}{0.9} = 5555$$

Dies per wafer

$$N_D = \frac{\pi r^2}{A_D} - \frac{\sqrt{2} \pi r}{\sqrt{A_D}} = 450$$

$$\# \text{ good dies} = 450 \times 0.65 = 292$$

$$\textcircled{a} \text{ IPC} = \frac{\frac{5555}{292} + 4^*}{0.85} + \frac{2 \times 10^6}{4 \times 10^6}$$

$$\text{IPC} = \$27.59$$

\* If test and packaging cost is taken as \$8, it is fine.

$$\textcircled{b} \text{ IPC reduces by 10\% } \text{IPC} = \$27.49$$

$$\textcircled{c} \# \text{ good dies} = 450 \times 0.8 = 360$$

$$\text{IPC} = \frac{\frac{5555}{360} + 4}{0.85} + 1 = \$23.85$$

better option




2a  $Y = \overline{A \cdot (B+C) \cdot (D+E) \cdot (F+G)}$

mathematical method

$$\overline{A(B+C)} + \overline{(D+E)(F+G)}$$

$$\overline{A(B+C)} + \overline{(D+E)(F+G)}$$

 
Top level OR implemented as inputs in a 4-input AND



②  $Y = A + F(B+C) + D(E+F)$

architectural method

-implement first with 2-input AND/OR gates and replace as you go

 



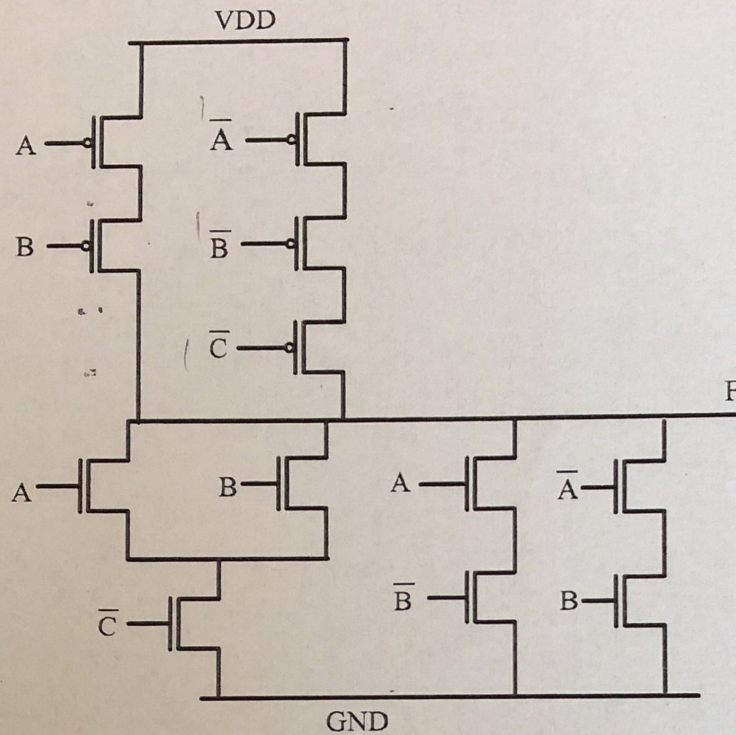


Figure 1: Logic circuit for problem 3

Problem 3. Determine the truth table and logic function for the circuit given in Figure 1.

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$F = \overline{A}\overline{B} + AB\overline{C}$$